

**Department of Computer Science and Engineering**  
**BRAC University**  
**CSE 260: Digital Logic Design**

**Experiment # 7**

*Design a circuit that outputs 2's complement of a 3 bit number using encoder & decoder.*

**IC: 74ls138 [decoder]; 74ls148 [encoder]**


*The Truth Table for 2's complement output:*

Inputs				Outputs				Active Low Output			Output line Connection	
Minterm	C	B	A	Minterm	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>	D2	D1	D0	Decoder	Encoder
0	0	0	0	0	0	0	0	1	1	1	0	0
1	0	0	1	7	1	1	1	0	0	0	1	7
2	0	1	0	6	1	1	0	0	0	1	2	6
3	0	1	1	5	1	0	1	0	1	0	3	5
4	1	0	0	4	1	0	0	0	1	1	4	4
5	1	0	1	3	0	1	1	1	0	0	5	3
6	1	1	0	2	0	1	0	1	0	1	6	2
7	1	1	1	1	0	0	1	1	1	0	7	1


**Report:**

The report should cover the followings

 1. Name of the experiment
2. Objective
3. Required Components and Equipments
4. Experimental Setup (i.e., diagram of the circuit)
5. Results and Discussions
  - a. Draw a circuit diagram with encoder and decoder that will output the 1's complement of 3 bit number.
  - b. Can you implement a code converter with encoder and decoder? If yes, how? If no, explain why not?



# 74138

 

# 74148

