

Lab Assignment - 1

Name: Ms Rodxy Tahmid

Sec: 09

ID: 20101021

Ans:

## ① Name of the Experiment:

Familiarization of Fundamental Logic Gates

## ② Objective:

■ To get familiarized with fundamental logic gates and demonstrate the input output relationship of 2-input AND (IC - 7408), OR (IC - 7432) and NOT (IC - 7404) gates by constructing their truth tables.

■ To get familiarized with logic gates like NAND (IC - 7400), NOR (IC - 7402), XOR (IC - 7486) and XNOR (IC - 74266).

## ③ Required Components and Equipments:

Logic Gates (AND gate, NOT gate, OR gate, XOR gate, XNOR gate, NAND gate, NOR gate),


Inputs (using logic state),

LEDs (Blue and other colors),


Power Source.

Ans no:


# ④ Experimental Setup :

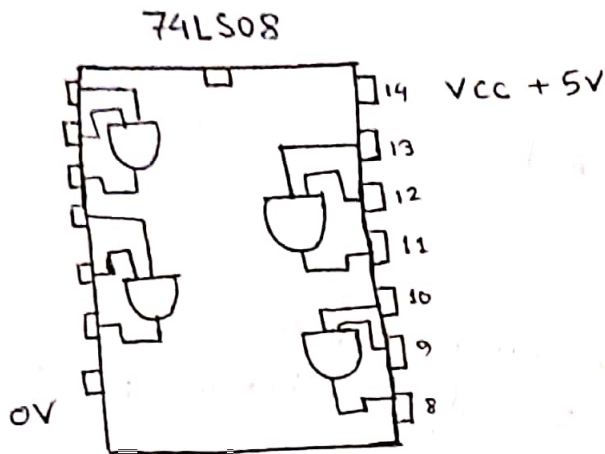


Pin layout of 7408 → AND

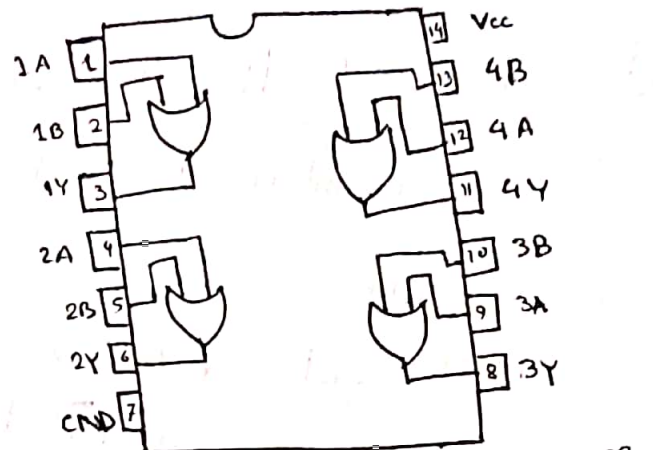


Pin layout of 7432 → OR

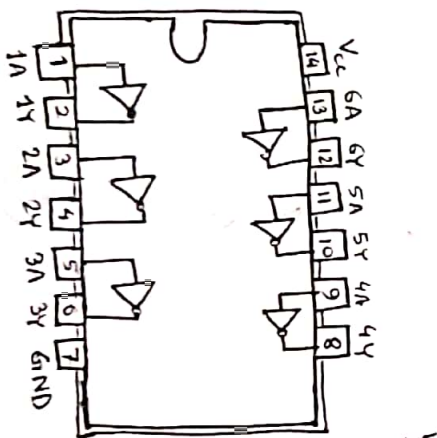


Pin layout of 7404 → NOT

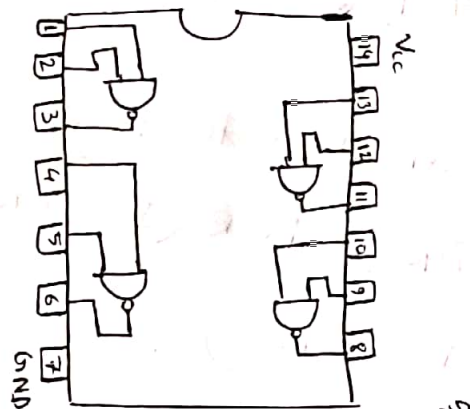


Pin layout of 7400 → NAND

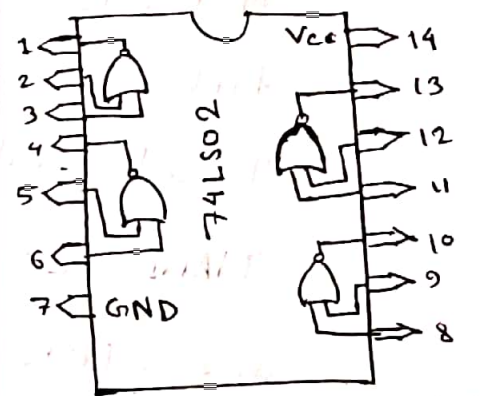

Pin layout of 7402 → NOR

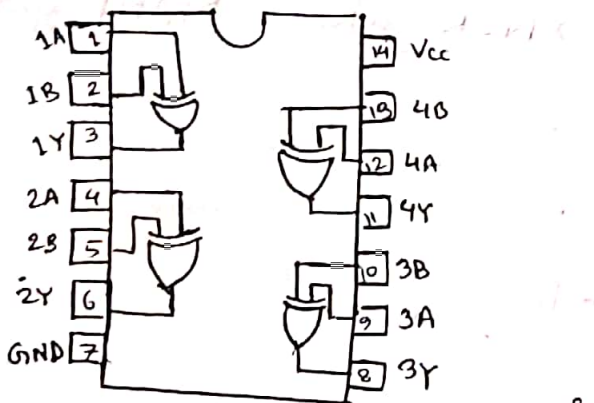

Pin layout of 7486 → XOR

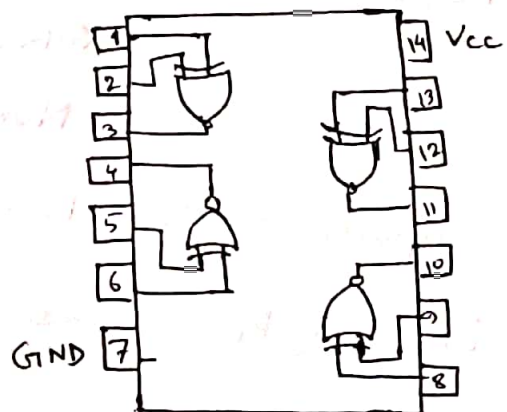

Pin layout of 74266 → XNOR

Ans. no.

(5) Results (Truth Table) and Discussion:

Results (Truth Table):

A	B	AND	OR	NAND	NOR	XOR	XNOR
0	0	0	0	1	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	1	0	0	0	1

Discussions:

My Outcomes were all as stated by the Truth Table: When 1, the LED light ~~the~~ turns blue, when 0, the LED light does not turn on i.e. switch it is off.

Limitation: Only turn on and off, no in-between switch, only 1 and 0.

Challenges: No Library is visible in Proteus Software unless administrator mode turned on.

What I learnt: Logic gates, How to use Proteus P.T.O

5) continuation.

④

Software, Different circuit materials (i.e. IC, Breadboard, Trainer Board) introduction, How the Logic Gates are implemented in Proteus, inner structures of different ICs (Integrated Circuits).