

Lab Assignment - 4

Name: Ms Rodney Tahmed

Sec: 09

ID: 20101021

Ans:

① Name of the Experiment:
Applications of Kmap method

② Objective:

- To investigate the rules of Kmap
- To gain experience working with practical circuits.
- To simplify a complex function using Kmap.

③ Required Components and Equipments

- offline {
1. AT-700 Portable Ant Analog / Digital Laboratory
 2. AND, OR, NOT, XOR IC.

1. Logic Gates (AND, OR, NOT, XOR)

2. Inputs (~~two~~ using logic state)

3. LEDs (Blue and other colors)

4. Power Source Ground.

④ Experimental St Setup.

⑤.1 Results (Truth Table).

Function:

1. $F(A, B, C, D) = \sum(1, 3, 9, 10, 13, 15)$ → minterm → 1.

AB \ CD	c'd' 00	c'd 01	cd 11	cd' 10	
00 → A'B'	0000	0001 (1)	0011 (1)	0010	1 ⇒ 0001
01 → A'B	0100	0101	0111	0110	3 ⇒ 0011
11 → AB	1100	1101 (1)	1111 (1)	1110	9 ⇒ 1001
10 → AB'	1000	1001 (1)	1011	1010 (1)	10 ⇒ 1010

$A'B'D$ (points to row 00)
 ABD (points to row 11)
 $B'C'D$ (points to column 01)
 $AB'CD'$ (points to column 10)

13 ⇒ 1101
 15 ⇒ 1111

Ans: $A'B'D + AB'CD' + ABD + B'C'D$

001 1010 111 1001
~~(Truth Table = 1)~~

(3)

Function:

$$2. F(A, B, C, D) = \sum (1, 4, 10, 15) + d(3, 5, 13, 14)$$

AB \ CD	C'D' 00	C'D 01	CD 11	CD' 10
00 → A'B'	0000	0001 (1)	0011 (X)	0010
01 → A'B	0100 (1)	0101 (X)	0111	0110
11 → AB	1100	1101 (X)	1111 (1)	1110 (X)
10 → AB'	1000	1001	1011	1010 (1)

$A'B'D$
 $1 \Rightarrow 0001$
 $A'BC'$ 4 $\Rightarrow 0100$
 ABD 10 $\Rightarrow 1010$
 $15 \Rightarrow 1111$

 $3 \Rightarrow 0011$
 $5 \Rightarrow 0101$
 $13 \Rightarrow 1101$
 $14 \Rightarrow 1110$

ACD'


$$\text{Ans: } A'BC' + ACD' + A'B'D + ABD$$

010 110 001 111

~~Truth Table 2.~~

Truth Table - 1

A	B	C	D	output
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

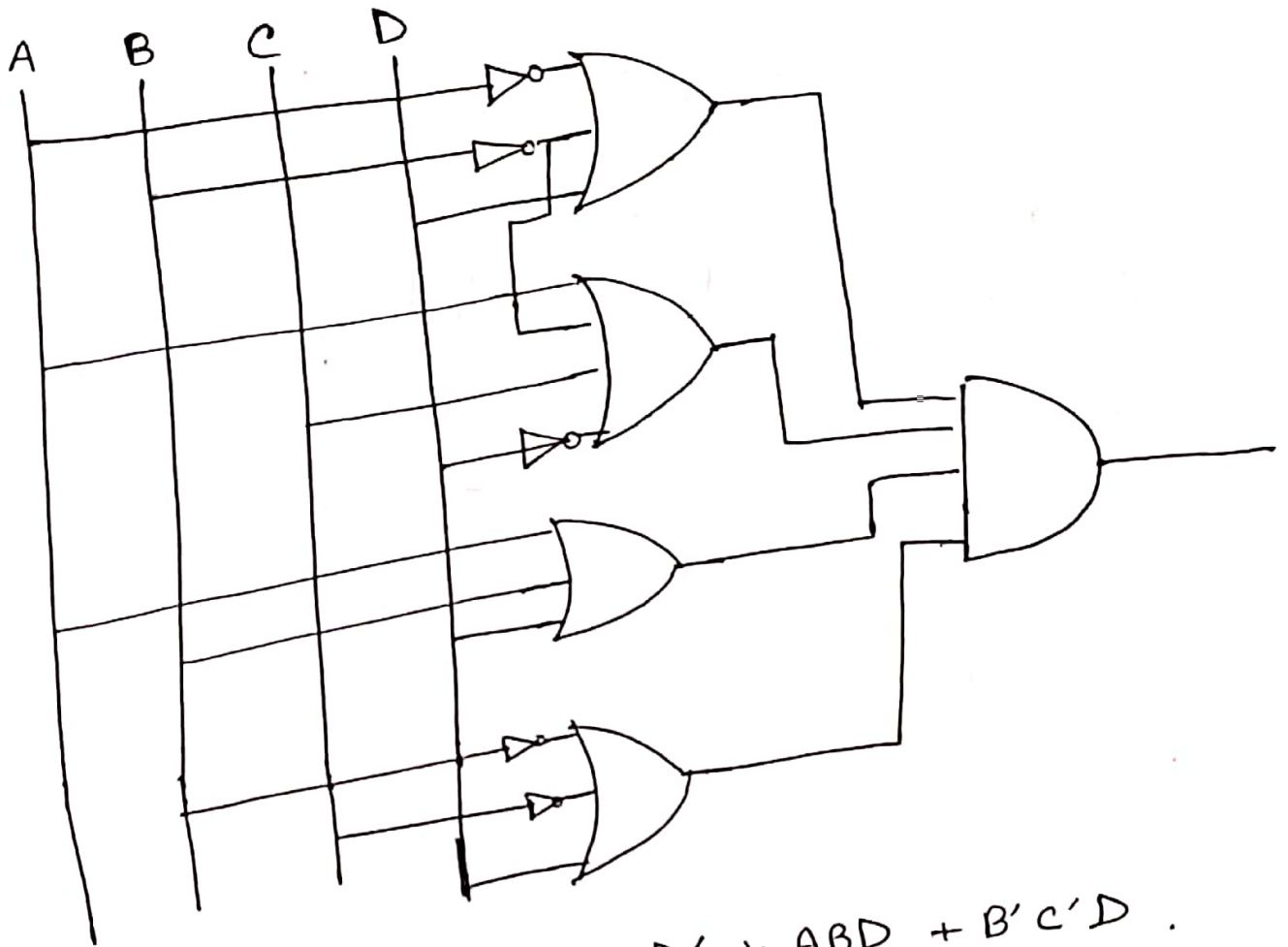


$$A'B'D + AB'CD' + ABD + B'C'D$$

Experimental Setup-1

Truth Table - 2

A	B	C	D	Output
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

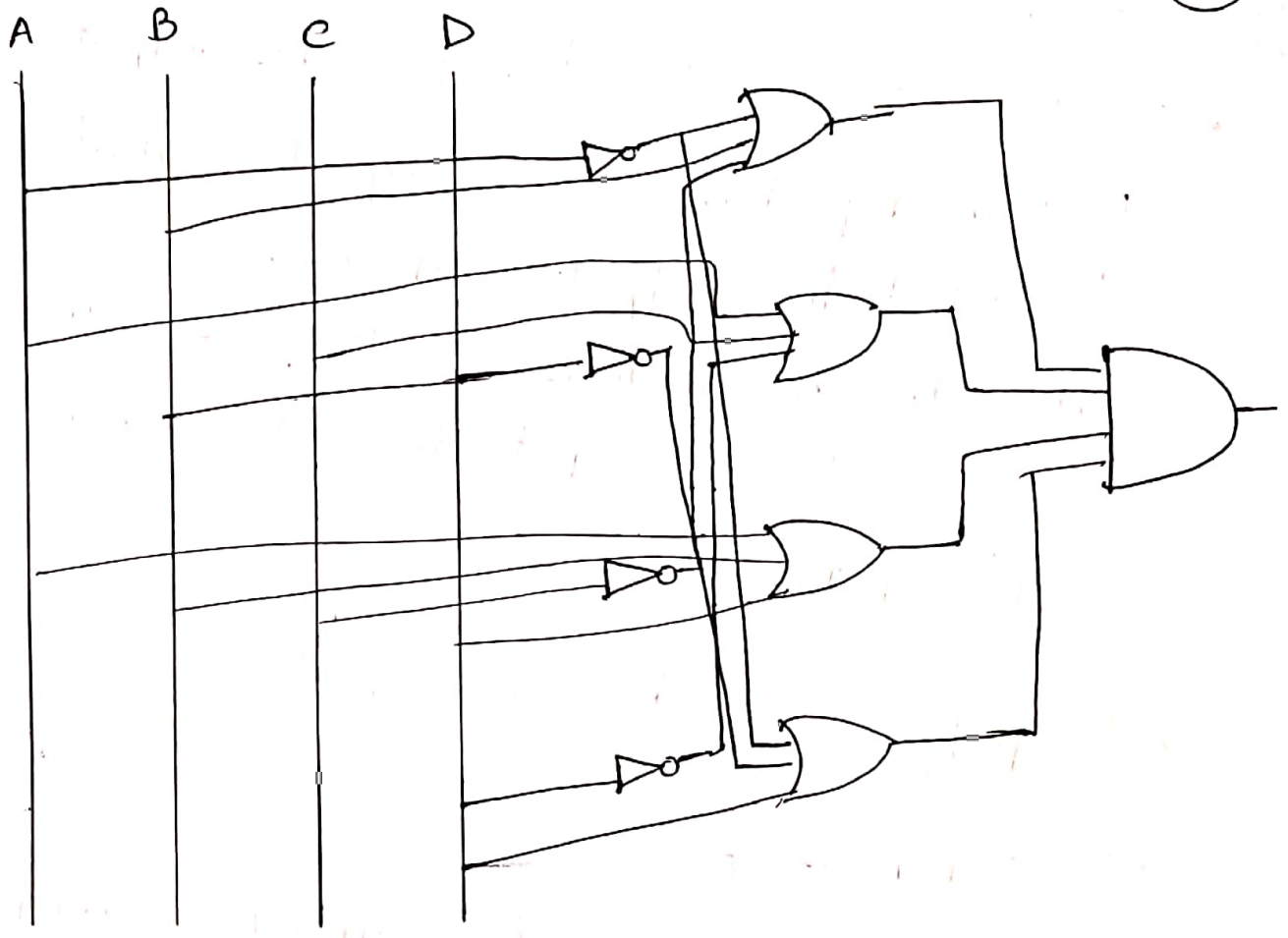

$$A'BC' + ACD' + A'B'D + ABD$$

Experimental Setup-2

5.2 Discussions:

- What is Boolean Equation for the output?
 Boolean Equation is the equation that suggests the what the output will be.
 Through the boolean equation, we can figure out the output from the given sets of input.

- Simplify the boolean Equation.

1) ~~$A'B'D = F$~~

$$F(A, B, C, D) = A'B'D + AB'CD' + ABD + B'C'D$$

2)

$$F(A, B, C, D) = A'BC' + ACD' + A'B'D + ABD$$