

Week-3

Cse 260

## Lab Assignment - 2

pg no: ①

Name: Ms Rodry Tahmid

Sec: 09

ID: 20101021

Ans:

① Name of the Experiment:

Applications of Boolean algebra

② Objective:

- To investigate the rules of Boolean algebra.
- To gain experience working with practical circuits
- To simplify a complex function using Boolean algebra.

③ Required Components and Equipments


- offline {
1. AT-700 Portable Analog / Digital Laboratory
  2. 7400 x 1

- online {
1. Logic Gates (NAND gates mainly)
  2. Inputs (using logic state)
  3. LEDs (Blue and other colors)
  4. Power Source.


Logic Gates (AND gate, NOT gate, OR gate, XOR gate, XNOR gate, NAND gate, NOR gate).

Ans no:


④ Experimental Setup :

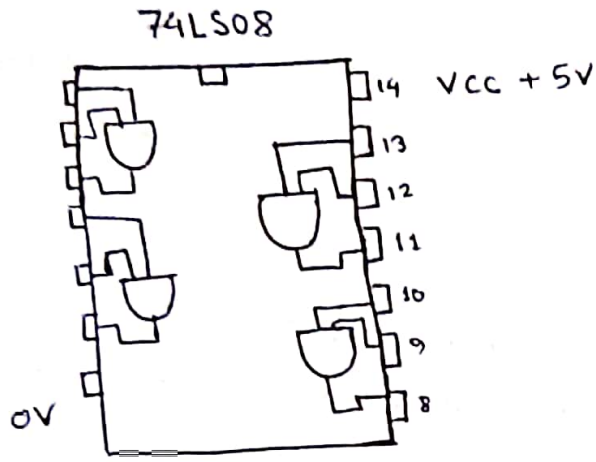


Pin layout of 7408 → AND

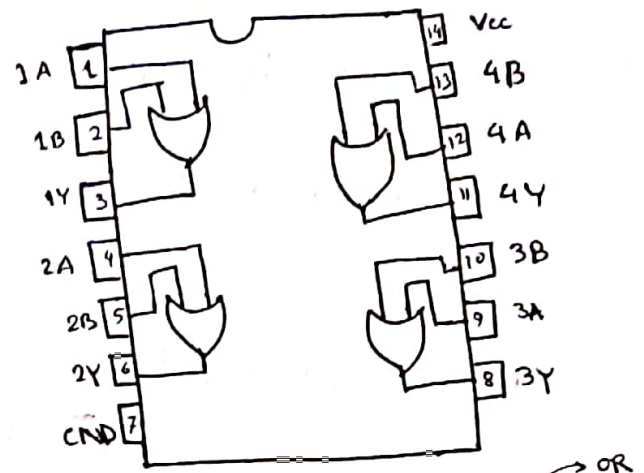


Pin layout of 7432 → OR

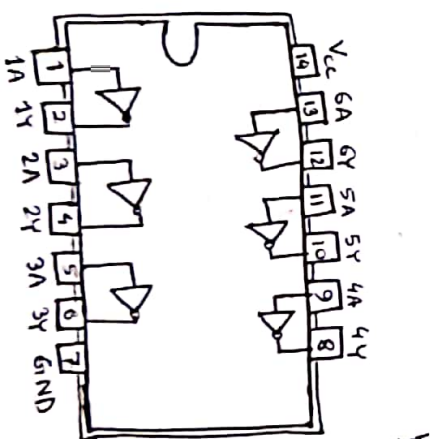


Pin layout of 7404 → NOT

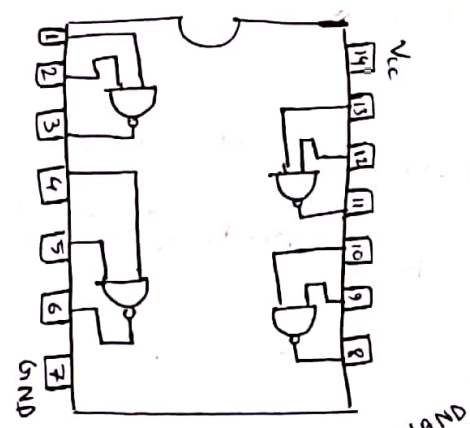


Pin layout of 7400 → NAND

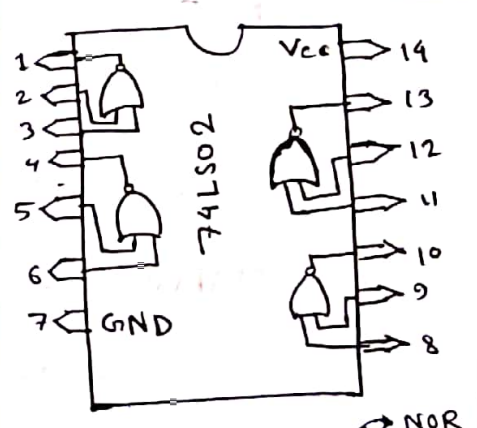

Pin layout of 7402 → NOR

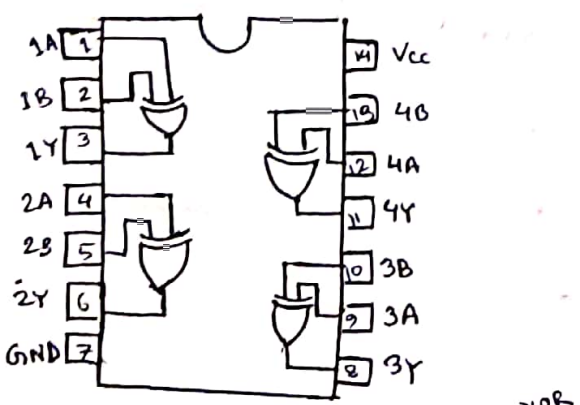

Pin layout of 7486 → XOR

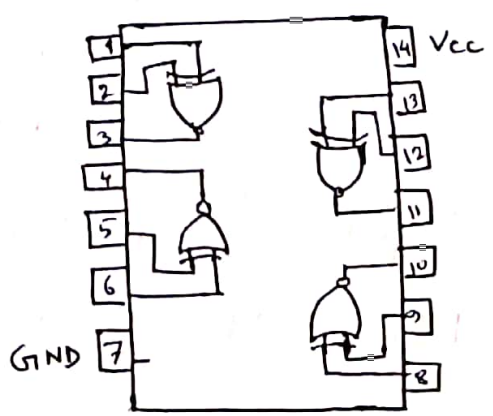


Pin layout of 74266 → XNOR

Ans no: Continuation.

(3)

#### ④ Experimental Setup:

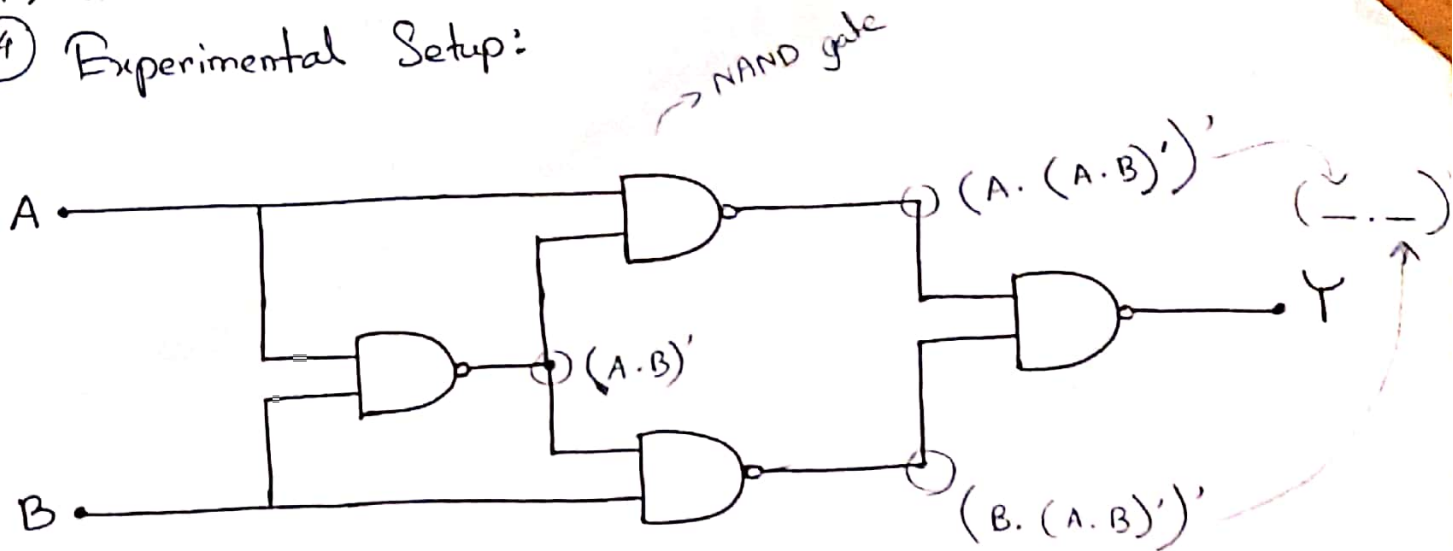

#### ⑤ Results (Truth Table) and Discussions:

Results (Truth Table):

Input 1 A	Input 2 B	Output Y
0	0	0
0	1	1
1	0	1
1	1	0

5 Discussion:

- What is the Boolean Equation for the output?

⇒ 1<sup>st</sup> NAND Gate:

$$(A \cdot B)'$$

2<sup>nd</sup> NAND Gate:

$$(A \cdot (A \cdot B)')'$$

3<sup>rd</sup> NAND Gate:

$$(B \cdot (A \cdot (A \cdot B)')')'$$

Y / Output :

$$((A \cdot (A \cdot B)')' \cdot (B \cdot (A \cdot B)')')'$$

- Simplify the Boolean equation

$$\Rightarrow ((A \cdot (A \cdot B)')' \cdot (B \cdot (A \cdot B)')')'$$

$$= ((A \cdot (A' + B'))' \cdot (B \cdot (A' + B'))')'$$

$$= ((A \cdot (A' + B'))' \cdot (B \cdot (A' + B'))')'$$

$$= ((AA' + AB')' \cdot (BA' + BB'))'$$

$$= ((0 + AB')' \cdot (A'B + 0))'$$

P.T.O

(5) → continuation.

$$= \left( (AB')', (A'B)' \right)'$$

$$= \left( (A' + (B')')', ((A')' + B')' \right)'$$

$$= \left( (A' + B)' \cdot (A + B')' \right)'$$

$$= \left( ((A')'(B)') \cdot A'(B')' \right)'$$

$$= (AB' \cdot A'B)'$$

$$= (AA' \cdot B'B)'$$

$$= (0 \cdot BB')'$$

$$= (0 \cdot 0)'$$

$$= 0$$



(6)

→ continuation.

$$\left( (A \cdot (A \cdot B)')' \cdot (B \cdot (A \cdot B)')' \right)'$$

$$= (A \cdot (AB)')' + (B \cdot (AB)')'$$

$$= A \cdot (A' + B') + B \cdot (A' + B')$$

$$= (AA' + AB') + (BA' + BB')$$

$$= (0 + AB') + (BA' + 0)$$

$$= AB' + BA'$$

$$= A \oplus B$$

$$(x' \cdot y')'$$

$$(x')' + (y')'$$

$$= x + y$$

$$(xy)' = x' + y' \quad \rightarrow \text{De Morgan}$$

$$2. (x +$$

$$x(y+z) = (xy) + (xz)$$

$$xx' = 0$$

$$x + x' = 1$$

- The circuit's function is identical to a single gate. Write down the name of that gate.
- ⇒ The name of that gate is XOR. The truth table from the simulation matches that with XOR truth table. Also, the function and diagram of the circuit is identical to XOR gate.